

SELEC CONTROLS

---

# INTERFACING MICROCONTROLLER

## **-HW Assignment 11-**

---

By : Ashwini Kumar Gupta

Dept. Of Electronics & Telecommunication

VES Institute of Technology, Chembur

July 19, 2018

# Contents

<b>1</b>	<b>Objective</b>	<b>1</b>
<b>2</b>	<b>Assignment Details</b>	<b>1</b>
<b>3</b>	<b>Design Considerations</b>	<b>1</b>
<b>4</b>	<b>Block Diagram</b>	<b>2</b>

## 1 Objective

To develop knowledge of selecting & Interfacing Microcontroller as per Application requirement.

## 2 Assignment Details

Select 'Renesas RL78 / G12 family ' Microcontroller suitable for following Application

1. Interface 12VDC, 20mA Buzzer (use HA6 Circuit )
2. Interface HONGFA Relay , 1Form A , 12 VdC coil supply , 10A Contact rating (use HA9 circuit)
3. Sense Healthiness of Mains AC Power supply , Mains supply > 100VAC is healthy condition ( use HA8 circuit)
4. Measure Sensor response , which O/P is in the range of 5mV to 100mV, amplified suitably for Single ended ADC of selected Microcontroller (use HA7 circuit)
5. Interface non isolated RS 485 port. (use TI make SN65HVD08)

## 3 Design Considerations

- controller Selection:
- The microcontroller should be able to handle analog voltage from the op-amp circuit, i.e. inbuilt ADC.
  - Should be able to understand TTL logic.
  - Low power consuming
  - should provide with at least 1 interrupt pin for RS485.
  - min of 2KB of ROM.
  - The Renesas RL78 / G12 family has a device R5F1026AASP suitable for this application.
- Crystal and capacitors:
- The for operating at 12MHz
  - Crystal ECS-120-8-33B-CZM-TR
  - the crystal capacitors required will be,

$$C_{l1} = C_{l2} = 2 * (C_l - C_p)$$

From data sheet we get  $C_l = 8 \text{ pf}$ ,  $C_p = 2 \text{ pf}$

$$C_{l1} = C_{l2} = 12 \text{ pf}$$

Reset – Reset pin is active low.

– the Reset pin will be connected to 3.3 V through a  $1\text{K}\Omega$  resistor and to GND through a push button.

I/P and O/P devices Buzzer \* It is an Output device requiring 1 GPIO with low current requirement.

\* attach Buzzer circuit to PIN 17.

\* Pin 17 is a PCLBUZ0 i.e a programmable pin dedicated to buzzer.

Relay \* It is an Output device requiring 1 GPIO with low current requirement.

\* attach Buzzer circuit to PIN 19.

Opto Isolator circuit \* It is an input circuit with TTL logic.

\* only requires Digital input pin.

\* assigning PIN 4/ PORT 40, since it is only input pin.

Op-Amp Circuit \* It is an input circuit with analog input.

\* Requires ADC pin.

\* Assigning pin 18 since it is an Analog Input pin (ANI3)

RS485 \* Requires a Digital Tx and Rx pin

\* Pin 15 is TxD0 for D (of RS485)

\* Pin 16 is RxD0 for R (of RS485).

\* Since RS485 is half duplex, we can control the RE and DE Pin from same interrupt pin of microcontroller.

\* Interrupt Pin 6 i.e INTP0 for RE and DE

Default \* Vss to GND

\* Vdd to 3.3V

\* set TTL analog voltage ref at  $AV_{refm}$  and  $AV_{refp}$

## 4 Block Diagram